

## FIGURE 10-10

Two-Stage, Voltage-Divider-Bias, Common-Emitter Amplifier

