

PROBLEM 10

Consider the following circuit diagram.

