

# EXAMINER'S PRACTICE QUESTIONS

Answers to the questions are given at the end of the book.

1. A circuit is shown in Figure 1.1. The circuit is connected to a 12 V DC source.

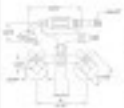


Figure 1.1