

QUESTION 2 (10%)

The following diagram shows a basic three-phase system.

Calculate the magnitude of the line current I_L and the real power P .

