

FIGURE 11.10

Block diagram of a power MOSFET amplifier.

