
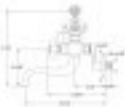


EXERCISES ON THE USE OF THE

INSTRUMENTS

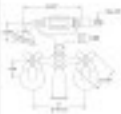1. Draw the circuit diagram of a Wheatstone bridge.



1