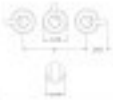


QUESTION

1. A circuit is shown in the diagram below. The battery has an emf of 12 V and negligible internal resistance. The resistors have resistances of 4 Ω, 6 Ω and 8 Ω.



ANSWER