

## EXPLORE

Identify the parts of the circuit and explain their functions.

