

KIRCHHOFF'S LAWS

For any closed loop in a circuit

