

PROBLEM 1

Consider the circuit shown below.



Figure 1