

# QUESTION 17

Which of the following is a correct statement about the following circuit?



ANSWER: A