

## PROBLEM 2.5. (10%)

Consider the circuit in Figure 2.5.1.

