

## PROBLEM 2.10

Find the Thévenin voltage and resistance for the circuit in Fig. 2.10.

