

HW4: HW1, 1.2, 3.5-6, 7 (2024)

Problem 1.1



- (a) Find the current i through the $100\ \Omega$ resistor.
- (b) Find the power dissipated in the $100\ \Omega$ resistor.
- (c) Find the power dissipated in the $200\ \Omega$ resistor.