



1. The circuit is complete when the switch is closed.

2. When the switch is closed, the bulb will glow.

3. The bulb glows because the circuit is complete and current flows through it.

4. The bulb will stop glowing if the switch is opened.

Diagram illustrating a simple circuit with a battery, a bulb, and a switch.



Diagram illustrating a simple circuit with a battery, a bulb, and a switch.