

# QUESTION 1

Consider the following circuit:

