

QUESTION

Two identical cells are connected in series with a variable resistor R and a voltmeter V as shown in the circuit diagram.

ANSWER

