

# QUESTION 20

Which of the following is a correct circuit diagram for a cell, a lamp and a variable resistor?

