

PROBLEM

1. A circuit is shown in the figure below. Find the current i through the $10\ \Omega$ resistor.

