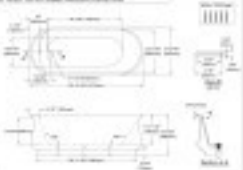


QUESTION

Figure 1 shows a circuit diagram of a lamp and a battery.



ANSWER

The circuit diagram shows a battery, a lamp, and a switch connected in a loop.