

QUESTION 10

Refer to the circuit diagram below. The circuit is initially in a steady state.

