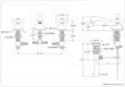


## QUESTION 1 (10 of 70 pts)

Answer the following questions about the circuit below.



1. The voltage across  $R_1$  is  $V_1$ .