

## QUESTION 2 (10)

The following diagram shows a circuit with two resistors and a battery.

