

QUESTION 10

Identify the correct circuit.

