

PROBLEM 11.10

Find the current i in the circuit.

