



QUESTION

What is the power dissipated in R_2 if $V_1 = 10V$ and $V_2 = 5V$?