

PROBLEM

Using the following circuit, determine the value of R_1 and R_2 .

