

## QUESTION 1.2 (10%)

Consider the following circuit diagram:

