

PROBLEM 13.61

Find the current i in the circuit.

