

QUESTION 13

Which of the following is a correct statement about the circuit shown?

