

# QUESTION 2 (10 MARKS)

Illustration of a simple circuit

