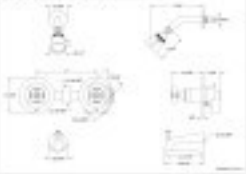


QUESTION

1. The following circuit is shown. What is the current through the 10 Ω resistor?



ANSWER

1. The current through the 10 Ω resistor is 10 A.