

# PROBLEMS 1.2.4 & 1.2.5

Two identical 100-ohm resistors are connected as shown.

