

# COMBINATION CIRCUIT

1. The circuit contains both series and parallel connections.

