

QUESTION 1 (4.7 MARKS)

Take a look at the circuit below for

