

# PROB 2.11

Consider the following circuit

