

PROBLEM 2-4.6.7 (25)

Two identical parallel-plate capacitors are connected as shown.

