

FIGURE 2.5.8.3

FIGURE 2.5.8.3. (a) Schematic diagram of a two-stage amplifier. (b) Frequency response plot showing magnitude and phase.

