

# QUESTION 2 (50%)

Consider the following circuit diagram:

