

QUESTION

Figure 1 shows a circuit diagram for a lamp and a motor.

The lamp is rated 12 V, 24 W.

