

QUESTION

Figure 1 shows a circuit diagram of a two-port network. The input port is terminated with a load impedance Z_L . The output port is terminated with a load impedance Z_T . The input voltage is V_i and the input current is I_i . The output voltage is V_o and the output current is I_o . The network is represented by a block diagram with a curved top edge on the left side.

