

CONTINUED

Draw the rest of the diagram to complete the circuit.



APPROXIMATELY 20 MIN