

QUESTION 1

Figure 1 shows a circuit diagram of a power supply circuit. The circuit is powered by a 240 V AC source. The circuit consists of a transformer, a diode bridge rectifier, a filter capacitor, and a load resistor.

