

QUESTION 14 (100)

Two identical parallel plate capacitors are connected in series to a battery.

