

## PROBLEM 1.3.8.8.7 (2014)

The figure shows a circuit with

