

PROBLEM 1

Consider the following circuit diagram.

