

## QUESTION 2 (10 MARKS)

Refer to the following circuit diagram.

