

FIGURE 3.10
Electrical circuit

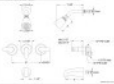


FIGURE 3.11 shows a circuit with a battery, a switch, and a motor. The circuit is completed by a bottom horizontal wire that connects the three light bulbs back to the battery.