

QUESTION 11 (10 MARKS)

The circuit below is a Wheatstone bridge circuit.

