

QUESTION

QUESTION: *Explain the following circuit diagram.*



ANSWER